

Sr. No: 11

Name: Soham Desai

Date: 25/01/22

Experiment 3

Aim: Realize Half adder and Full adder


LO & Statement : LO: 2) Analyze and design combinational circuits

Software Requirements: Logisim software

Theory:

Half Adder

 - The half adder is an example of a simple, functional digital circuit built from two logic gates.
- The half adder adds to one-bit binary numbers (A,B).
- The output is the sum of the two bits (S) and the carry



Half adder truth table

A	B	Sum	Carry-Out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B \text{ (Exclusive OR)}$$

$$C = A.B \text{ (AND)}$$

For carry

B \ A	0	1
0	0	0
1	0	1

$$\text{Carry} = AB$$

For Sum

B \ A	0	1
0	0	1
1	1	0

$$S = AB + \bar{A}B + A\bar{B}$$


Sr. No: 11

Name: Soham Desai

Date: 25/01/22

Full Adder

 - The full adder accepts two inputs bits and an input carry and generates a sum output and an output carry.
- The full-adder circuit adds three one-bit binary numbers (C_{in} , A , B) and outputs two one-bit binary numbers, a sum (S) and a carry (C_{out}).
- The full-adder is usually a component in a cascade of adders, which add 8, 16, 32, etc. binary numbers.



HALF ADDER TRUTH TABLE

Inputs			Outputs	
A	B	C – IN	Sum	C – Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

For S:

\overline{A}	$\overline{B}\overline{C}$	$\overline{B}C$	$B\overline{C}$	BC
\overline{A}		1		1
A	1		1	

$$S = A \oplus B \oplus C_{in}$$

For C_{out} :

\overline{A}	$\overline{B}\overline{C}$	$\overline{B}C$	$B\overline{C}$	BC
\overline{A}			1	
A		1	1	1


$$C_{out} = AB + BC_{in} + C_{in}A$$

Sr. No: 11

Name: Soham Desai

Date: 25/01/22

Output:

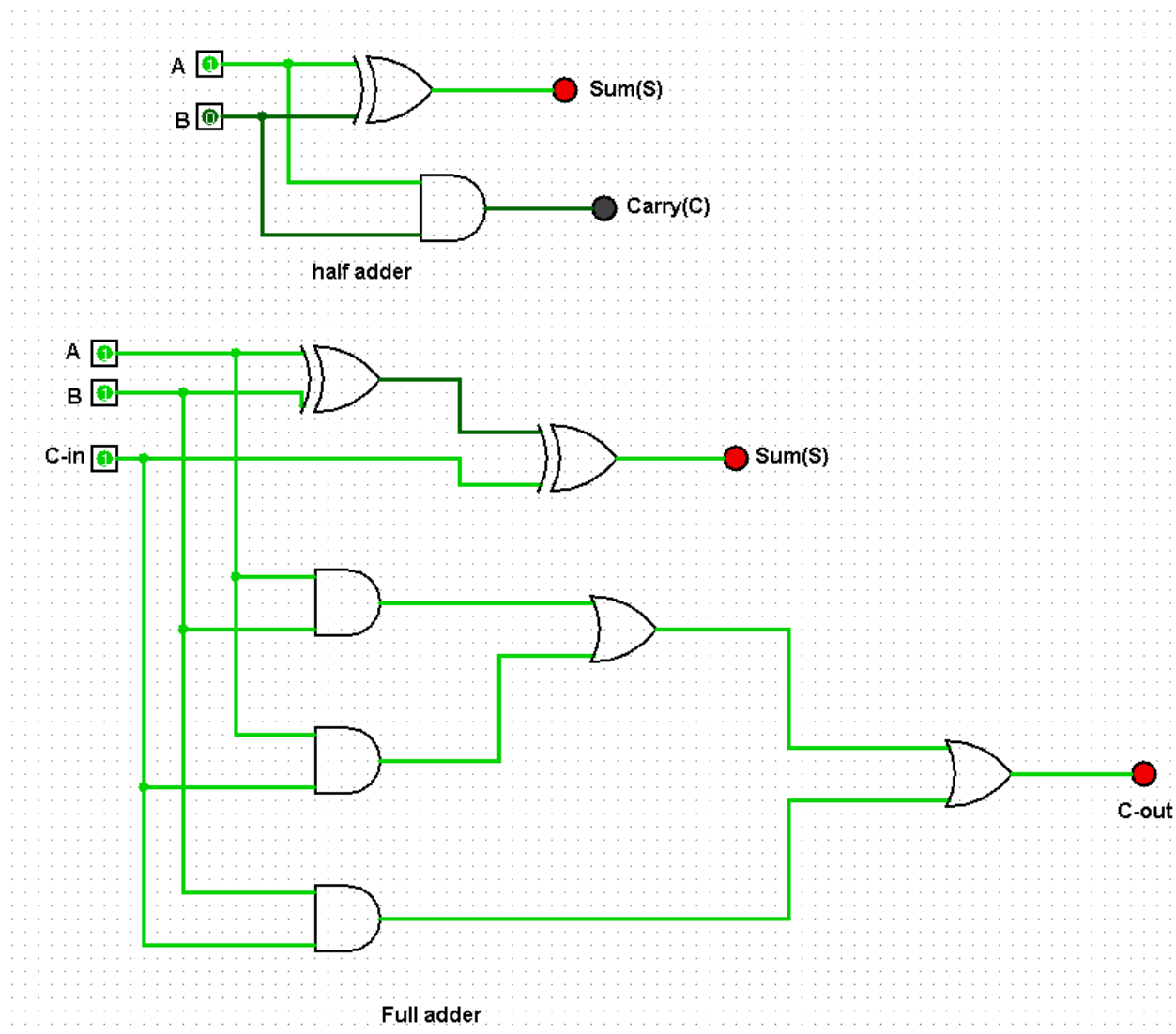

Conclusion:

The half adder and full adder is working as expected